


Consider a buck-dc-dc converter with the following specifications: $f_{sw} = 100 \text{ kHz}$, $V_d = 24 \text{ V}$, $6 \text{ V} < V_0 < 9 \text{ V}$ and $R = 10 \text{ ohms}$. Compute the value of L required for the converter to operate with CCM under all cases.

The ranges of load current and duty cycle are: $0.6 \text{ A} < I_o < 0.9 \text{ A}$ and $0.25 < D < 0.375$.


The converter operates with V_d constant and variable D , therefore one can use the graph shown in Fig. 7.6. To achieve CCM, the minimum load current ($I_{o\min}$) has to be larger than the boundary current (I_{oB}). $I_{o\min} = 0.6 \text{ A}$ and occurs when $D = 0.25$.

In this case $L \geq 37.5 \text{ uH}$

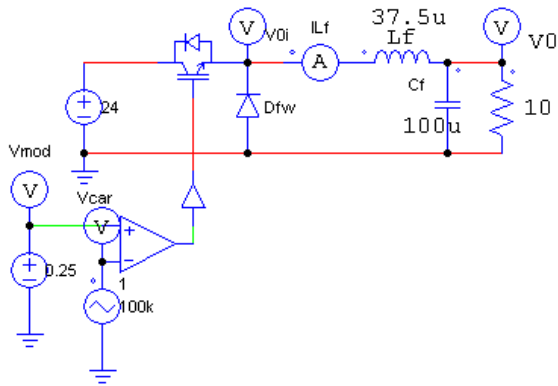
The PSIM simulation file, using a filter capacitor of 100 u and a time step of 0.1 us , looks like:



Simulation results:

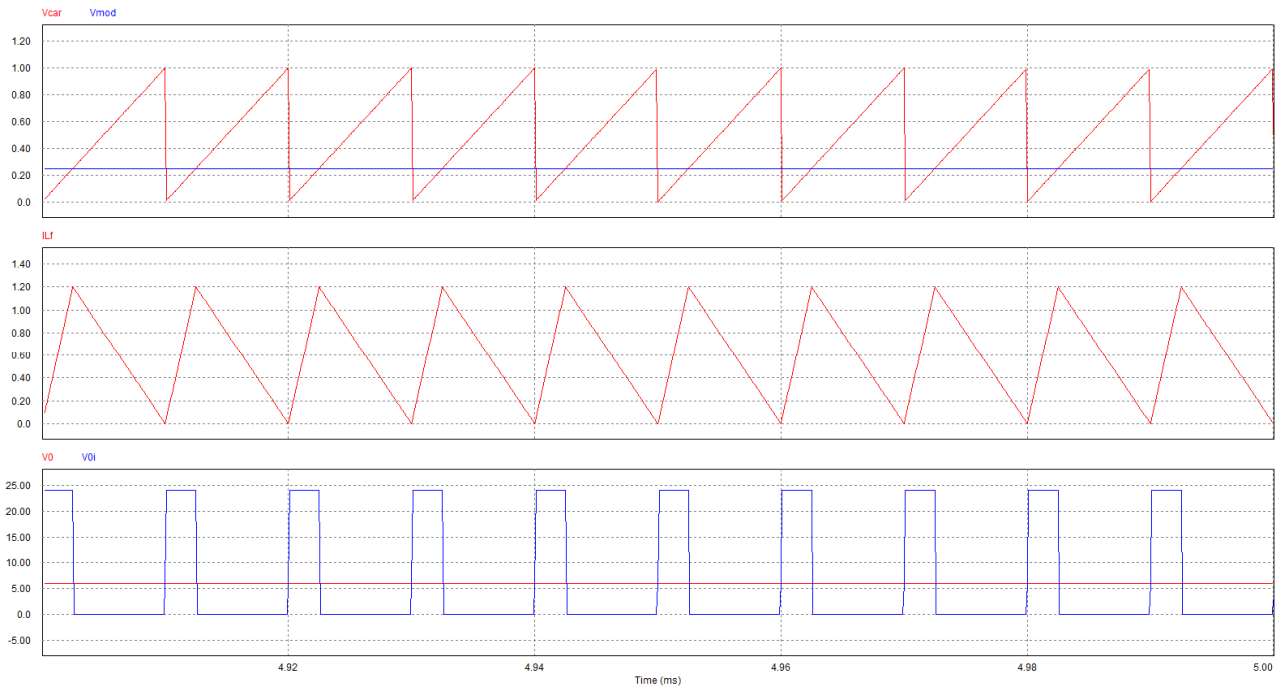


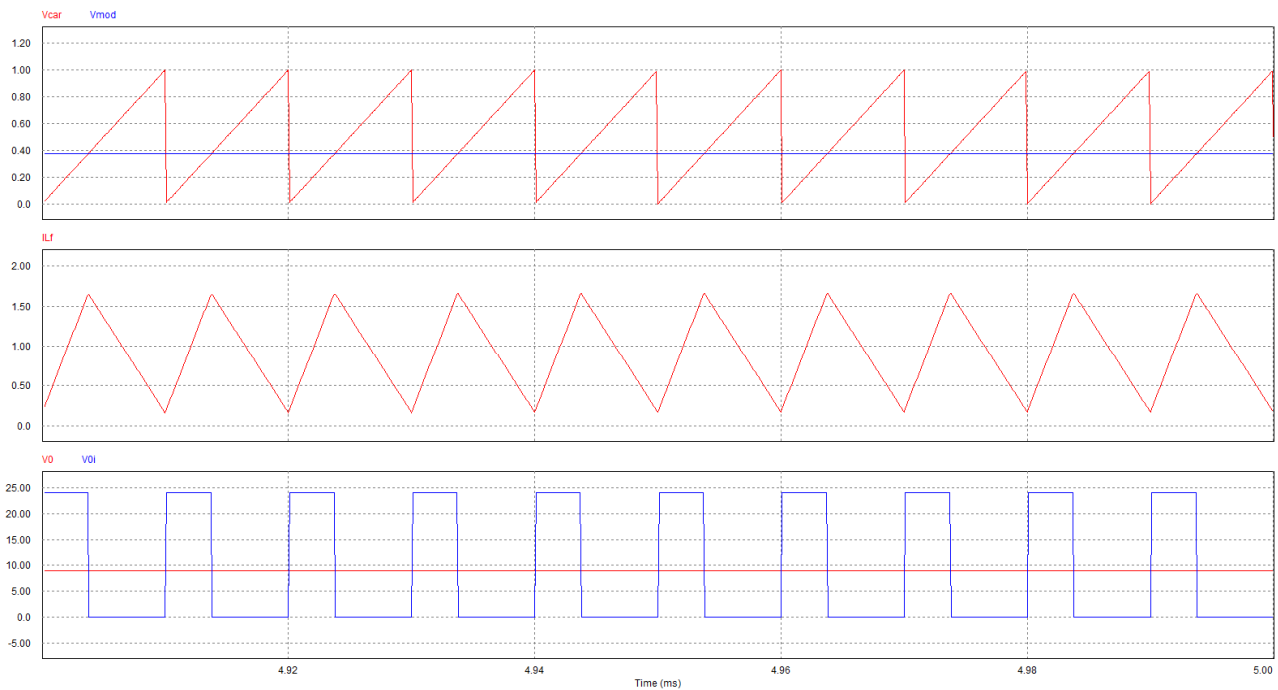For the case one wishes to have an output voltage equal to 9V, the simulation results are:



Since this was not the critical case, the current is always above 0 A.

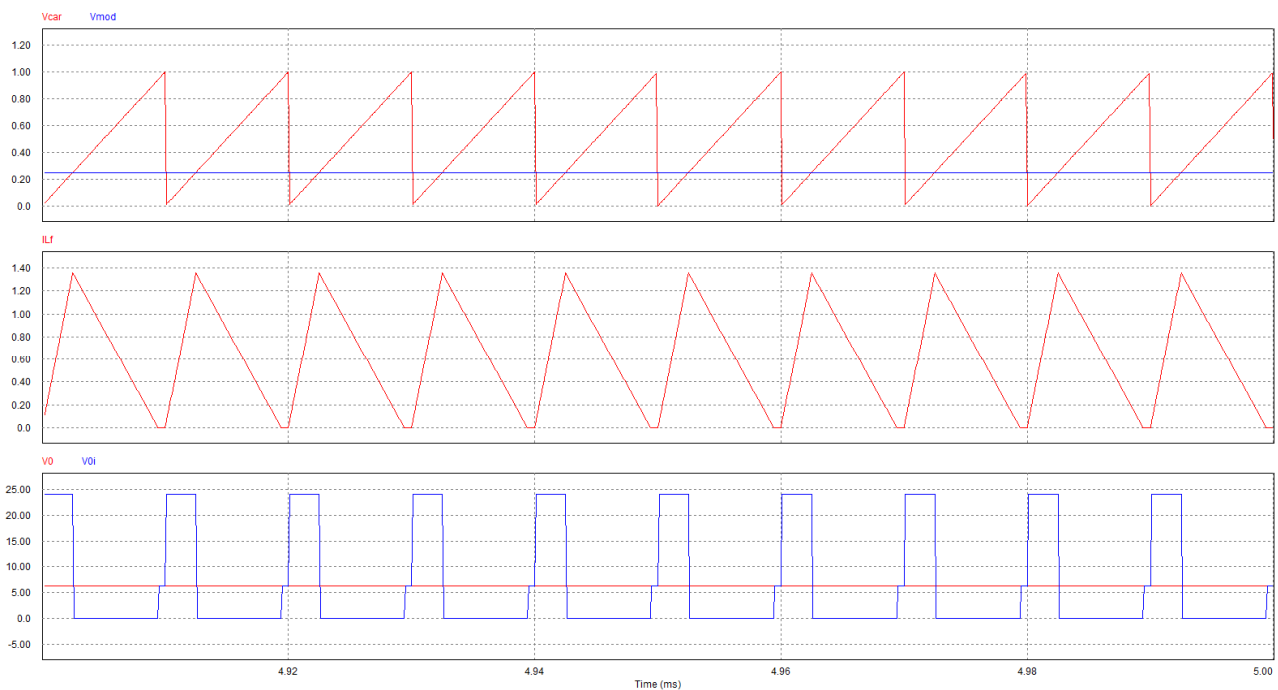If a smaller inductor, say 32.5 μH had been used for the critical case ($D = 0.25$ and $I_o = 0.6$ A), the simulation results would be:



There one sees that the system indeed operates with DCM and the output voltage of the converter (V_{0i}) now presents 3 levels. It is equal to V_0 while the inductor current is zero. The value of V_0 is now 6.38 V, bigger than the 6V obtained with relation $D V_d$ which is only valid for CCM.

Additional information in section 7-4-3 of the textbook, not discussed in this course.